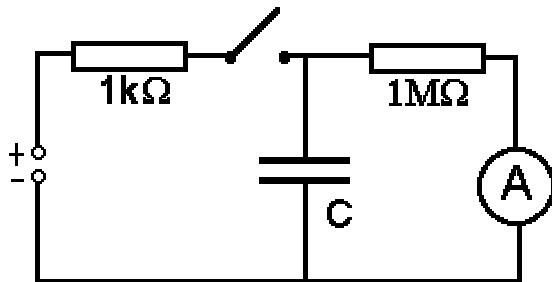


Versuch: Entladen eines Kondensators

Aufbau:



Beobachtung:

t in s	0	4	8	12	16	20	24
I in μA	50	43	35	29	24	20	17

t in s	28	32	36	40	44	48	52
I in μA	14	12	10	9	7,5	6	5